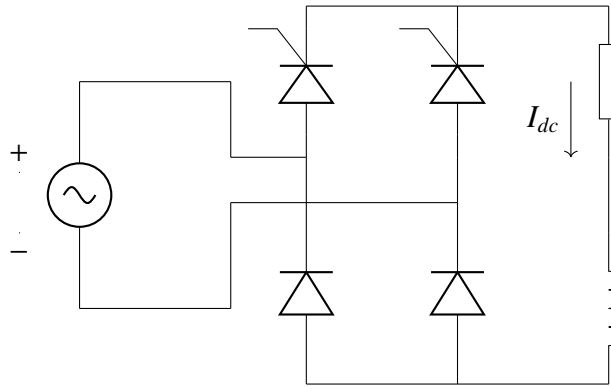


GATE: EE - 59.2022

EE23BTECH11013 - Avyaaz*

Question: For the ideal AC-DC rectifier circuit shown in the figure below, the load current magnitude is $I_{dc} = 15$ A and is ripple free. The thyristors are fired with a delay angle of 45° . The amplitude of the fundamental component of the source current, in amperes, is _____ (Round off to 2 decimal places). (GATE 59 EE 2022)




Solution:

Parameter	Description	Value
I_{dc}	Load current	15A
α	Firing angle	45°





TABLE 1

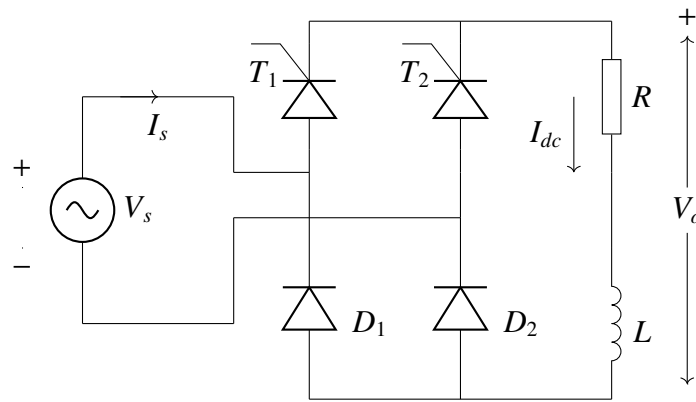A symmetrical single phase semi converter is shown below,



The Fourier series representation of supply current is given by:
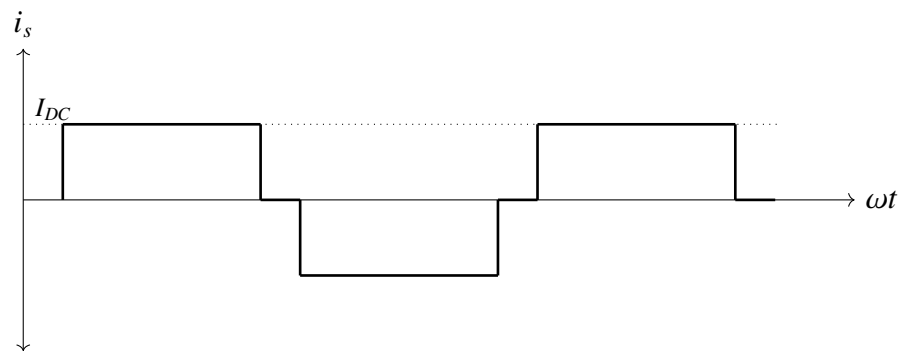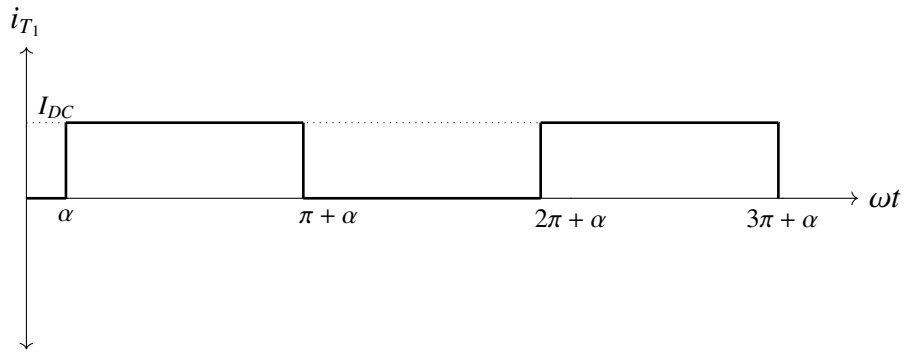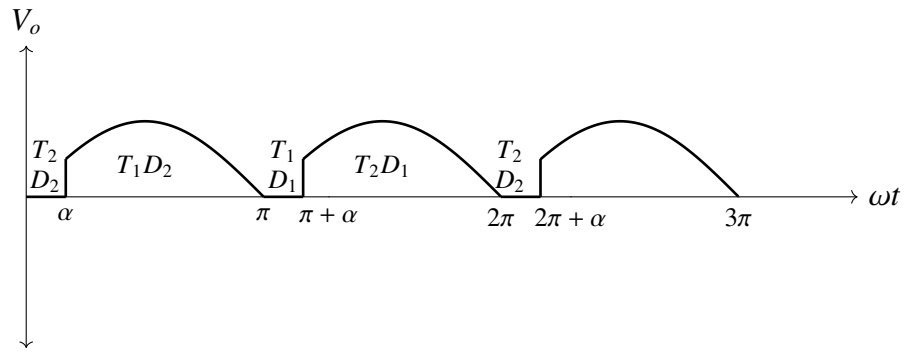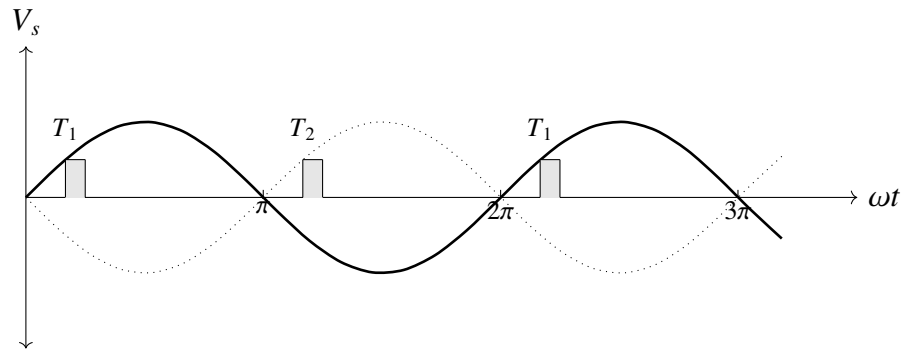
$$I_s(t) = \sum_{n=1,3,5,\dots}^{\infty} \frac{4I_{dc}}{n\pi} \cos \frac{n\alpha}{2} \sin \left(n\omega t - \frac{n\alpha}{2} \right) \quad (1)$$



From Table 1:

$$(I_{s_1})_{peak} = \frac{4I_{dc}}{\pi} \cos\left(\frac{\alpha}{2}\right) \quad (2)$$

$$= \frac{4 \times 15}{\pi} \times \cos \frac{45^\circ}{2} \quad (3)$$

$$= 17.64A \quad (4)$$